

CprE 381 – Computer Organization and Assembly-Level Programming

Proj-A Report

Lab Partners Jacob Vaughn
 Nickolas Mitchell


Section / Lab Time 1/4:10-6:00

Submit a typeset pdf version of this on Canvas by the due date. Refer to the highlighted language in the Proj-A instructions for the context of the following questions.

[Part 0] With your project group members, create a list of best practices / tips for designing, compiling, and testing VHDL modules based on your experiences so far with these labs, both working individually and as a group.

Our best practices and tips for designing, compiling, and testing VHDL modules include giving meaningful names to entities and signals, using useful comments to explain different parts of our code, perform various tests using the simulation tool, and compile often.

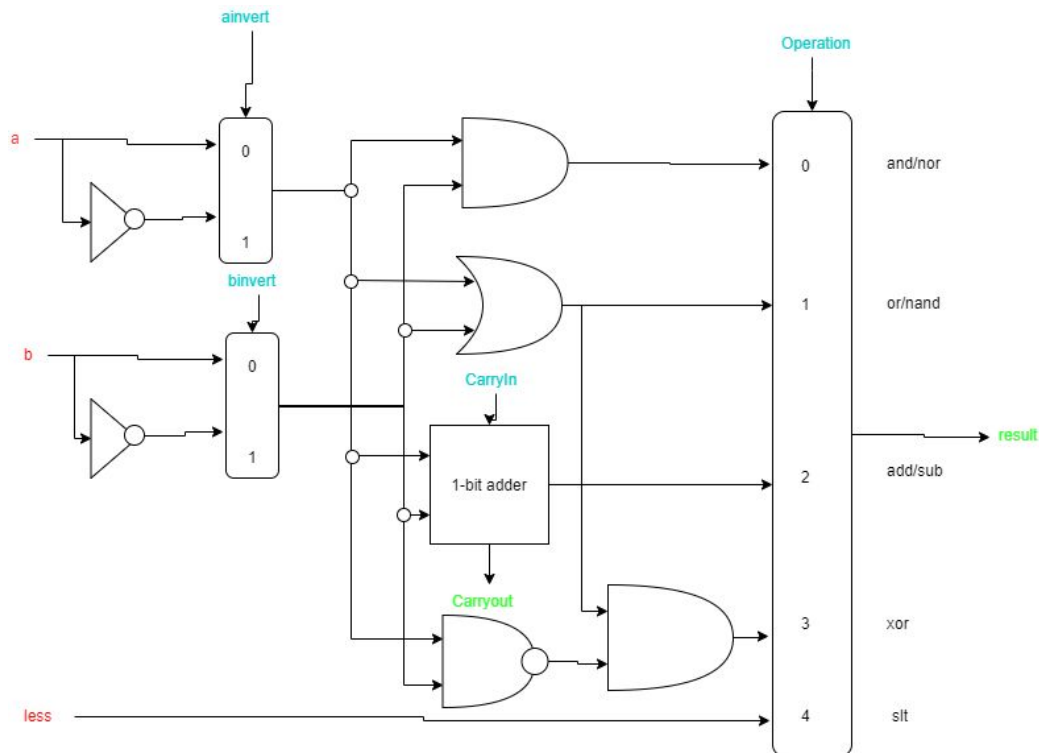[Part 1 (a)] Draw a schematic for a 1-bit ALU that supports the following operations: add/sub (both signed and unsigned), slt, and, or, xor, nand, and nor. What are the inputs and outputs that are needed?



Input's are *a*, *b*, *less*, and then control's for *ainvert*, *binvert*, *carryin*, and *Operation* (*3bit*). The output is going to be from the operation mux: *result* and a *Carryout* from the adder.

[Part 1 (b)] In your project writeup, describe your design in terms of the VHDL coding style you chose and the control signals that are required.


For our design we are using mostly structural coding with a little data flow mixed in. We have used this coding style mostly due to the fact this is what we are most comfortable working with. Our design makes use of 6 control bits (3 to select the operation to output, 2 to select between a and b or not a and b, and 1 carry-in bit).

[Part 1 (c)] Describe how the execution of the different operations corresponds to the Modelsim waveforms in your writeup.

ainvert, *binvert*, *Carryin*, *Operation-3bit*

000000 : AND
000001 : OR
000010 : Add
000011 : xor
011100 : slt
110000 : NOR
110001 : NAND
011010 : Sub

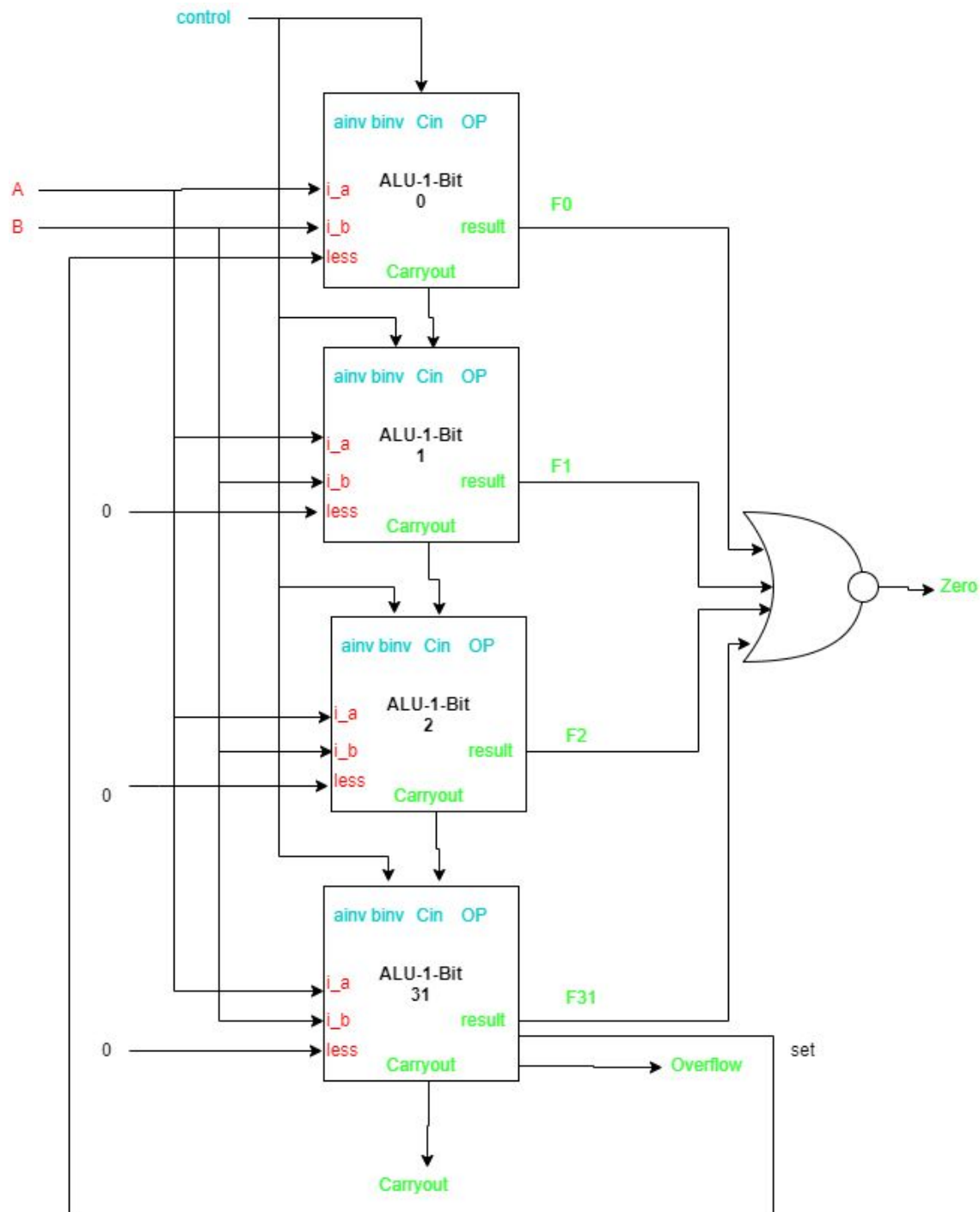[Part 2 (a)] Draw a simplified schematic for this 32-bit ALU. Consider the following questions: how is Overflow calculated? How is Zero calculated? How is slt implemented?



[Part 2 (b)] In your writeup, describe what challenges (if any) you faced in implementing this module.

I thought when doing a generate that it would act like a process loop, but it is actually just setting up the circuit aka generating it and then running everything. After we understood this it was easy to make the slt functionality.

[Part 2 (c)] Describe how the execution of the different operations corresponds to the Modelsim waveforms in your writeup.

[illegible]

Here is one of my sets of test as you can see i start with a 2 operation which is Add where s_A is added to s_B and output to s_F

Next I did a 1A operation which is subtraction

then 0 operation which is and AND operation of the two inputs

1C which is a slt and this works both when a is bigger than b and vice versa

next a 01 op which is an OR

then 03 which is XOR

and finally a 30 which translates to NOR or the inputs.

these are some of my test cases to give an example of operands.

[Part 3 (a)] Describe the difference between logical (srl) and arithmetic (sra) shifts. Why does MIPS not have a sla instruction?

In MIPS, the logical right shift (srl) always shifts bits to the right cutting off any bits which shift past the 0th bit and adds 0's in the most significant bits up until the 31st bit.

The arithmetic shift right (sra) performs exactly like a logical shift right if the most significant bit is a 0. When the most significant bit is a 1 instead of a 0, the arithmetic shift right shifts 1's. MIPS does not a shift left arithmetic (sla) instruction because signed values will never shift 1's to the left. Signed values only shift 1's to the right.

[Part 3 (b)] In your writeup, briefly describe how your VHDL code implements both the arithmetic and logical shifting operations.

Firstly, to implement the shift right logical operation our code simply consists of 5 32bit 2:1 multiplexers which shift to the right by 1bit, 2bits, 4bits, 8bits, 16bits respectively using concatenation and 5 bit control signal which determines how many bits to shift.

Next, our shift right arithmetic operation starts out by taking saving the most significant bit to a 1 bit signal then that bit is used to shift right with the previously mentioned multiplexers.

[Part 3 (c)] In your writeup, explain how the right barrel shifter from part b) can be enhanced to also support left shifting operations.

To shift right, our code flips the input bits and performs a right logical shift then the result is flipped back again to represent a shift left operation. Our code utilizes a 2 bit control signal and with else statements to select which of the three shifts our code will perform.


'00' <= arithmetic shift right


'01' <= logical shift right

'10' <= Shift left

/right_left_shifter/f...	32h800F000	7070F0F0						8000F000			
/right_left_shifter/c...	5h1F	04								1F	
/right_left_shifter/c...	2h2	X		1		0		2	0		2
/right_left_shifter/o...	32h00000000	07070F0F					070F0F00	F8000F00		00000000	
/right_left_shifter/e...	0										
/right_left_shifter/s...	32h00078000	7070F0F0					0F0F0E0E	8000F000		00078000	
/right_left_shifter/s...	32h0001E000	7070F0F0					0F0F0E0E	8000F000		0001E000	
/right_left_shifter/s...	32h00001E00	07070F0F					00F0F0E0	F8000F00		00001E00	
/right_left_shifter/s...	32h0000001E	07070F0F					00F0F0E0	F8000F00		0000001E	
/right_left_shifter/s...	32h000DF0001	7070F0F0					0F0F0E0E	8000F000		000F0001	
/right_left_shifter/s...	32h000DF0001	0F0F0E0E						000F0001			
/right_left_shifter/o...	32h00000000	F0F0E0E0					070F0F00	00F0001F		00000000	
/right_left_shifter/t...	32h00000000	07070F0F					00F0F0E0	F8000F00		00000000	
/right_left_shifter/s...	32h00078000	38387878					07878707	C0007800		00078000	
/right_left_shifter/s...	32h0001E000	1C1C3C3C					03C3C383	E0003C00		0001E000	
/right_left_shifter/s...	32h00001E00	07070F0F					00F0F0E0	F8000F00		00001E00	
/right_left_shifter/s...	32h0000001E	0007070F					0000F0F0	FFF8000F		0000001E	
/right_left_shifter/s...	32h00000000	000000707					000000F0	FFFFF800		00000000	

 [Part 4(b)] Justify why your test plan is comprehensive. Include waveforms that demonstrate your test program is functioning.



 

Our test in the test bed includes all of the operations of the ALU that needed to be tested for functionality. It also includes loading and storing to make sure they still work with the new ALU lastly it includes test cases with the shift registers testing edge cases where signed and unsigned values would matter. Everything works with the test cases given. The problem we were running into before was with the register file not being able to be read because of a work file being named incorrectly. Other than that hiccup everything went smoothly leading to a fully functional ALU and simplified MIPS processor.

[Part 5(c) BONUS] Justify why your test plan is comprehensive. Include waveforms that demonstrate your test program is functioning.

[Feedback] You must complete this section for your lab to be graded. Please complete each column separately for each team member; I expect it to take roughly 10 minutes (do not take more than 20 minutes).

i. How many hours did you spend on this lab?

Task	During Lab time		Outside of lab time	
Team Initials	JV	NM	JV	NM
Reading lab	0	0.25	0.5	0.5
Pencil/paper design	0.5	0.5	0	0.5
VHDL design	1.5	1	3	2
Assembly coding	0	0	1	0
Simulation	1	0.5	1	1
Debugging	1	1	4	4
Report Writing	0	0.5	0.5	1
Other	0	0.25	0	0

Total	4	4	9	9
-------	---	---	---	---

- ii. If you could change one thing about the lab experience, what would it be? Why?
 If we could change one thing about this lab, we would have spent more time before this lab began testing the components used in previous labs. Having components from pervious labs which don't work correctly have left us scrambling to finish project A.
- iii. What was the most interesting part of the lab?
 The most interesting part of this lab was figuring out how to modify our ALU to support several other MIPS instructions. We thought this was a cool process in general and hope we will be able to condense instructions into single components in future labs.